

# DSD LAB

## LAB 1

### Q1)

Write Verilog code to describe the following functions

$$f1 = ac' + bc + b'c'$$

$$f2 = (a + b' + c)(a + b + c')(a' + b + c')$$

Check whether f1 and f2 in question 1 are functionally equivalent or not.

#### Source Code :

```
module q1(a, b, c, f1, f2);
```

```
input a, b, c;
```

```
output f1, f2;
```

```
not(a1, a);
```

```
not(b1, b);
```

```
not(c1, c);
```

```
and(fa1, a, c1);
```

```
and(fb1, b, c);
```

```
and(fc1, b1, c1);
```

```
or(f1, fa1, fb1, fc1);
```

```
or(fa2, a, b1, c);
```


```
or(fb2, a, b, c1);
```

```
or(fc2, a1, b, c1);
```

```
and(f2, fa2, fb2, fc2);
```

```
endmodule
```

#### Output Waveform:

 

From the graph it is clear that f1 and f2 are functionally equivalent.

**Q2)**

Simplify the following functions using K-map and implement the circuit using logic gates. Write Verilog code and simulate the circuit

a)  $f(A,B,C,D) = \Sigma m(1,3,4,9,10,12) + D(0,2,5,11)$

b)  $f(A,B,C,D) = \Pi M(6,9,10,11,12) + D(2,4,7,13)$

**a)**

The expression  $\Sigma m(1,3,4,9,10,12) + D(0,2,5,11)$  simplifies to the following expression:

$$F = BC'D' + B'D + B'C$$


### Source Code:

```

module q2a(a, b, c, d, F);
input a, b, c, d;
output F;
assign F = (b & ~c & ~d) | (~b & d) | (~b & c);
endmodule

```

### Output Waveform:

 

**b)**

The expression  $f(A,B,C,D) = \Pi M(6,9,10,11,12) + D(2,4,7,13)$  evaluates to:

$$F = (A' + B + D')(A' + B + C')(A + C' + D)(B' + C + D)$$


### Source Code:

```

module q2b(a, b, c, d, F);
input a, b, c, d;
output F;
assign F = (~a | b | ~d) & (~a | b | ~c) & (a | ~c | d) & (~b | c | d);
endmodule

```

## Output Waveform:

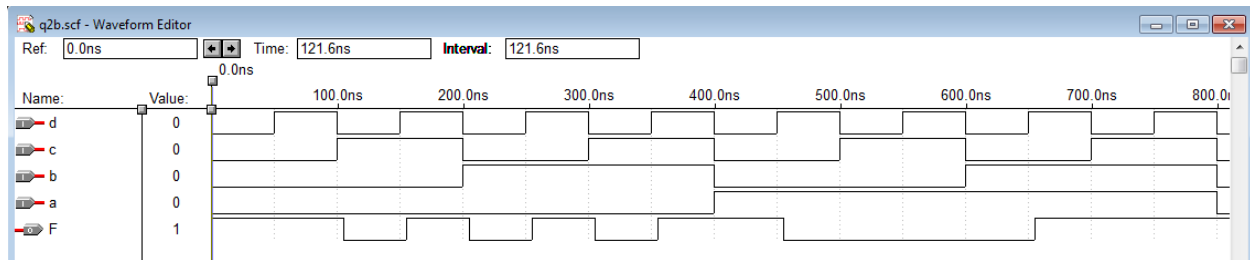

### Q3)

Minimize the following expression using K-map and simulate using only NAND gates.  
 $f(A,B,C,D) = \pi M(2,6,8,9,10,11,14)$

The expression  $f(A,B,C,D) = \pi M(2,6,8,9,10,11,14)$  simplifies to:  
 $F = A'C' + A'D + BC' + BD$

### Source Code:

```
module q3(a, b, c, d, F);  
input a, b, c, d;  
output F;
```

```
assign F = ~(~(~a & ~c) & ~(~a & d) & ~(b & ~c) & ~(b & d));  
endmodule
```

## Output Waveform:

